

# THE MARCH OF TELEVISION

## **RADIO NEWS**

**March  
25 Cents**

**Radio Surgery  
Triple-Twin Tube  
Newest Set Tester**



**Televising  
the  
"Races"**

LE-0-111072 EY 31





not interfere with each other. The cap on top of the tube is connected to the grid of the first section; both plates are brought out to the base of the tube.

Incidentally, the plate voltage for both sections is 250 volts. Although a direct coupling is used, the plates are at the same potential.

### The Circuit Employed


Let us first discuss the working of the triple-twin tube as an amplifier. The circuit is shown in Figure 1. In the cathode lead—that is, in the plate circuit—there is a resistance  $R_2$  and an audio-frequency choke across it. The audio-frequency choke serves to provide a low resistance path for the direct-current component of the plate current. This does away with the loss of voltage in the coupling resistor  $R_2$ . The direct-current component then goes through the choke, but the signal, at audio frequency, finds the choke a too high impedance path and most of it will flow through the resistance  $R_2$ . For all practical purposes, we can say that the signal flows through  $R_2$  and this is the "load." In the circuit of Figure 1 this load is connected across the cathode and grid of the second section of the tube.

The bias to the first tube is provided by the voltage drop across the resistance  $R_4$ , which carries the plate current of both the second and first tube. A small additional bias is obtained by the voltage drop across the choke. If we made the grid return (of the first section) to ground, as is usual in amplifier circuits, there would be a large resistance in the grid circuit. To provide a low-impedance return path to the cathode for the signal, the condenser  $C_1$ , of 2 microfarads, is provided. This again necessitates the resistance  $R_1$ , for without it the load would be short-circuited.

The signal is then amplified in the first section and develops an a.f. potential across the load which is connected to the grid and cathode of the next tube. However, the bias of the second tube is much smaller than that of the first. The grid of this tube, therefore, goes "positive" and it will draw current. One of the merits of the circuit is that this fact does not cause any distortion, for the circuit is so designed as to compensate for the additional current, which is drawn by the grid circuit.


We assume that the reader understands the causes for distortion in the ordinary coupled circuits, if the grid goes positive. In that case, current is drawn, and during that part of the cycle the impedance of the grid circuit changes and so the applied voltage, during that part of the cycle, drops, thus distorting the signal.

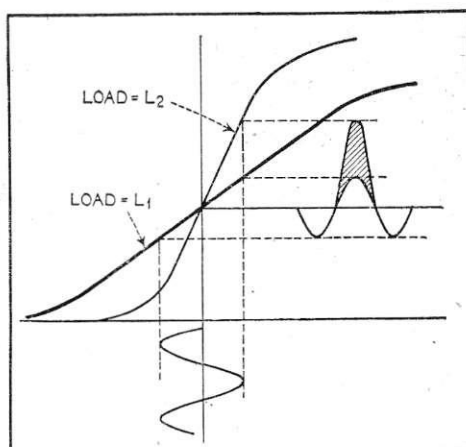Let us draw the dynamic characteristic of a tube for a certain load  $L_1$  (see Figure 2). This represents the grid-voltage, plate-current curve for the tube (first section) when  $R_2$  is the



GRID CURRENT COMPENSATION

Figure 2. Dynamic characteristics for single tube at different loads. When a signal is impressed on the grid, the tube automatically varies its load so that a steepening characteristic is obtained for lowered load impedances

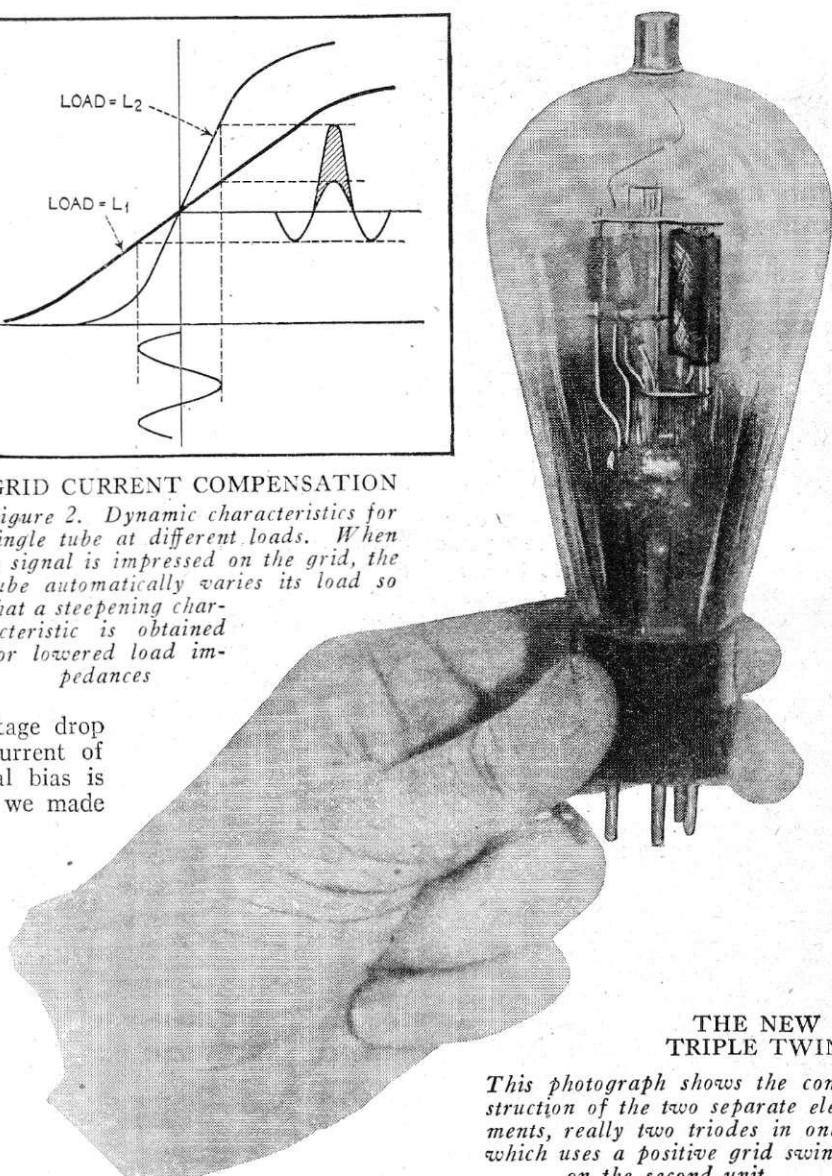


### THE NEW TRIPLE TWIN

This photograph shows the construction of the two separate elements, really two triodes in one, which uses a positive grid swing on the second unit


load and the grid of the second section is still negative. Then at a certain point the grid becomes positive and makes the load impedance less. The dynamic characteristic then becomes steeper for this new load,  $L_2$ , and it intersects the first one at the point where the conditions change.

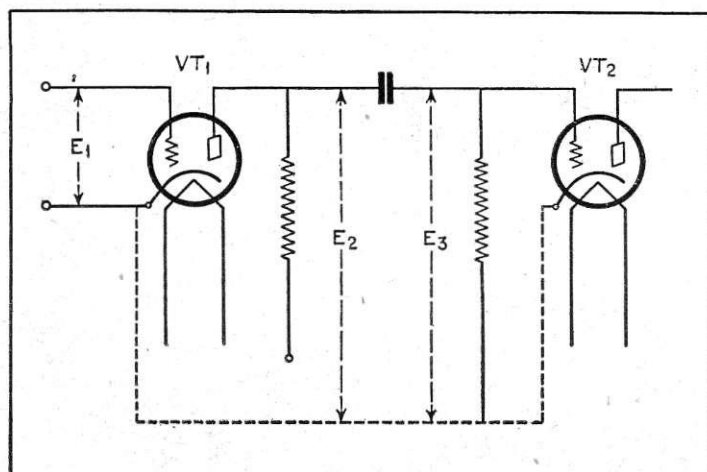When we now consider a sinusoidal signal, which is being impressed on the grid, we see that the part of the cycle which causes the second grid to go positive falls on the characteristic of  $L_2$  and that part causes a larger variation in plate current, thus providing additional current for (Continued on page 802)



RESISTANCE-COUPLED PHASE RELATIONS

Figure 3. (Left) In standard resistance-coupled amplifiers the voltage  $E_2$  between the plate and cathode is 180 degrees out of phase when the signal voltage  $E_1$  is impressed between the grid and cathode. The voltage  $E_3$  is approximately 70 degrees advanced over  $E_2$  and about 110 degrees retarded behind  $E_1$ . Figure 4. (Right) This is the electrical circuit diagram for using the triple twin tube as a combined detector and audio amplifier.

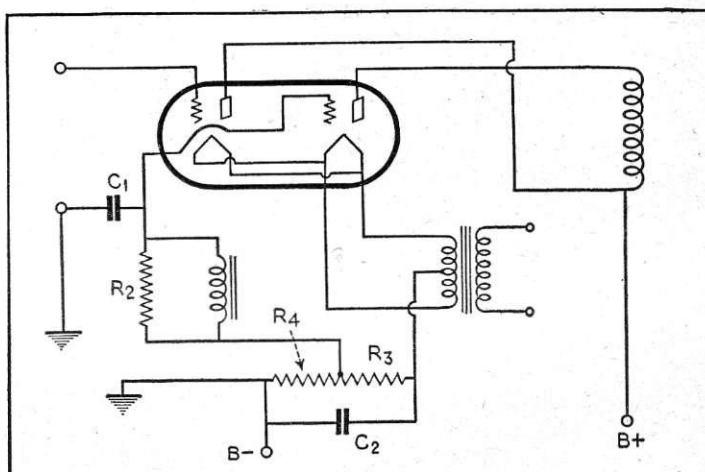

DETECTOR AND OUTPUT CIRCUIT



**It's free:  
—this story of  
Centralab  
Fixed Resistors**

Thousands of copies have already been distributed to servicemen, amateurs and engineers. Get your copy now . . . and this well-illustrated, informative booklet is free for the asking. Use the coupon . . . today.

**Note:** Effective Jan. 1, 1932, new low price on Centralab Volume Controls now make these Replacement Units more popular than ever.

**Centralab**

**MAIL COUPON NOW**

CENTRAL RADIO LAB.  
929 E. Keefe Ave., Milwaukee, Wis.

Please send me your FREE booklet, "A BAPTISM OF FIRE" ☐.

Am enclosing 25c for your "VOLUME CONTROL GUIDE" ☐.

Name .....

Address .....

City ..... State .....  
Radio News

# What Is the Triple-Twin Tube?

(Continued from page 761)

the grid current. In other words, this increase by the change in the characteristic is just equal to the current the grid draws and the current through the load R2 remains the same: a sinusoidal wave.

Of course, the compensation will not be exactly equal to the grid current unless the tube is carefully designed to do just that. Also, the load L2 varies during this half cycle; the more grid current, the lower the load, and we really would have to draw a whole family of curves.

## The Phase Relation

So far we have only spoken about the compensation for grid current during a part of the cycle and did not consider whether the compensation came at the right part of the cycle. In order for it to do so, the plate current will have to be in phase with the voltage on the grid of the next tube. It is, in this particular circuit, but not in any of the other conventional circuits. If such a compensation was attempted with a standard hook-up, it would come at the negative half of the cycle and would make matters worse instead of better.

In Figure 3 is shown a standard resistance-coupled circuit. We all know that when during the positive half of the cycle the control grid of VT1 becomes less negative, the plate current will increase, and during the negative half it will decrease. The plate current is then in phase with the incoming signal on the grid.

## Operating Characteristics

When the plate current increases, the voltage drop across the resistance R increases and the remaining part of the B-voltage is what is left for the tube, so the plate voltage drops when the plate current increases and it increases during the negative half of the cycle. The plate voltage, from cathode to plate, is opposite in phase to the grid voltage and the incoming signal. The voltage across the load R1 is in phase with the signal, but we do not usually connect that to the grid circuit of the tube. The latter circuit is generally coupled to the plate and cathode. The condenser in the resistance-coupled amplifier brings an additional phase difference. But it should be seen that, whatever type of coupling is used, the voltage on the grids of the two tubes will be out of phase and no compensating could be accomplished with the above described method.

## Compensating Current

Now let us look at Figure 1. Here the voltage across the load R2 is in phase with the signal applied on the grid of the first tube. This signal is directly connected across the grid and the heater of the second tube, and therefore the voltages on the first and second grid are in phase. This shows that the increase in plate current, due to a change in the load, will come at the right time to compensate for the grid current.

It was found that R3 was necessary to eliminate hum. This one tube, with the circuit shown in Figure 1, is all that is needed for a phonograph pick-up. The output in the plate of the tube will be as much as the dynamic speaker can handle, if not too much.

## The Detector Circuit

According to data supplied to us by the Cable Tube Company, the triple-twin tube will deliver 4½ watts to the speaker when used as a C-bias detector. To obtain this output the carrier has to be 10 volts.

In Figure 4 is shown the hook-up for the

detector circuit. The difference between this and the amplifier circuit is mainly in the values of the components. The condenser C1 has now become .0005 mfd., which is a low impedance for the radio-frequency component. The signal across the load—that is, the audio component—which is applied to the second section of the tube, finds this condenser a high-impedance path. Therefore, the grid return can be connected to ground without short-circuiting the load.

In this case the resistor R4 is larger, so as to get the proper bias on the input section. The bias on the output section remains the same as in the amplifier.

In this case the grid will go positive again and there will be just the right amount of compensation, as described above, because of the shifting of the characteristic as soon as the grid draws current.

## Other Applications

One of the great problems in television is to design an audio amplifier with a nearly straight-frequency characteristic. At present the audio-frequency band seems to go up to 50 kc. only, but soon this is expected to be increased. The frequency characteristic is substantially straight from 30 to 50,000 cycles. This should be a great help for designers of television receivers.

## Photo-Cell Amplifiers

The plate circuit of the 295 tube draws 50 ma. The variation in plate current for a given change in grid voltage is larger than that of most tubes generally used for photo-electric cell amplifiers.

It seems to the writer that the triple-twin tube increases the possibilities of industrial applications of the photo-electric cell. With the greater amplification possible, relays do not have to be so delicate and can be made to control the power circuit directly.

In the sound-film industry, also, this new amplifier should find wide application. It would greatly simplify the construction of the amplifier in the projection booth, with less chance of breakdown, not to speak of the reduction in cost.

## Engineering Data

By courtesy of the Cable engineers, we give below some of the characteristics which were obtained by experiments in their laboratory:

Filament voltage.....	2.5 volts a.c.
Filament current.....	.4 amperes
Plate voltage, first section.....	250 volts
Plate voltage, output section.....	250 volts
Mutual conductance, first section.....	1150
Mutual conductance, output section.....	3700
} approximately	
Plate current.....	50 ma.
Grid bias input.....	6 volts
Plate impedance.....	4000 ohms
Recommended load impedance.....	4000 ohms
Maximum undistorted output.....	4.5 watts

The minimum harmonic distortion is 5% at 4000 ohms. It is 8% at 2000 ohms and at 9800 ohms. This is the second and third harmonic combined. Note that the minimum distortion is at 4000 ohms, which is the impedance needed for maximum power output. There is no need for designing special transformers, as with the pentode. A standard output transformer designed for -45 type tubes or for -50 type tubes will do. It must be able, however, to stand the 50 ma. plate current.

In the diagram of Figure 1, R1 = 1 megohm, R2 = 12,500 ohms, R3 = 70 ohms, R4 = 210 ohms, approximately.